

- ANALOGUE ELECTRONIC

Active Filter



Introduction

- Filters are circuits that are capable of *passing signals within a band* of frequencies while *rejecting or blocking* signals of frequencies *outside this band*. This property of filters is also called “frequency selectivity”.
- Filter can be passive or active filter.

Passive filters: The circuits built using RC, RL, or RLC circuits.

Active filters : The circuits that employ one or more op-amps in the design an addition to resistors and capacitors

Advantages of Active Filters over Passive Filters

- Active filters can be designed to provide required gain, and hence no attenuation as in the case of passive filters
- No loading problem, because of high input resistance and low output resistance of op-amp.
- Active Filters are cost effective as a wide variety of economical op-amps are available.

The header features five circles arranged horizontally. The first, third, and fifth circles are solid light blue. The second and fourth circles are white with a light blue outline. The word "Applications" is written in a bold, blue, sans-serif font, centered over the second and third circles.

Applications

- Active filters are mainly used in communication and signal processing circuits.
- They are also employed in a wide range of applications such as entertainment, medical electronics, etc.



Active Filters

➤ There are 4 basic categories of active filters:


- 1. Low-pass filters**
- 2. High-pass filters**
- 3. Band-pass filters**
- 4. Band-reject filters**

➤ Each of these filters can be built by using op-amp as the active element combined with RC, RL or RLC circuit as the passive elements.


BASIC FILTER RESPONSES

Low-Pass Filter Response

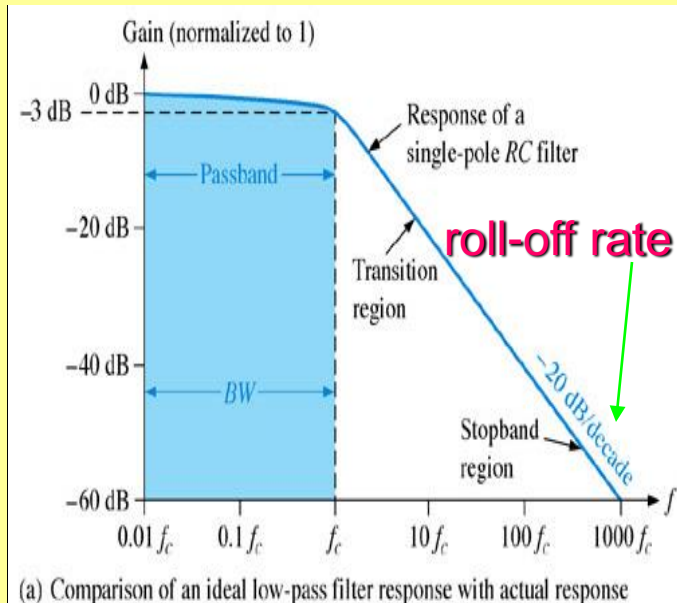
- A **low-pass filter** is a filter that passes frequencies from 0Hz to critical frequency, f_c and significantly attenuates all other frequencies.



Actual response

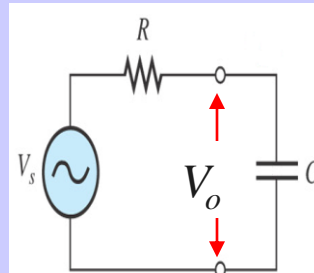

(b) Basic low-pass circuit

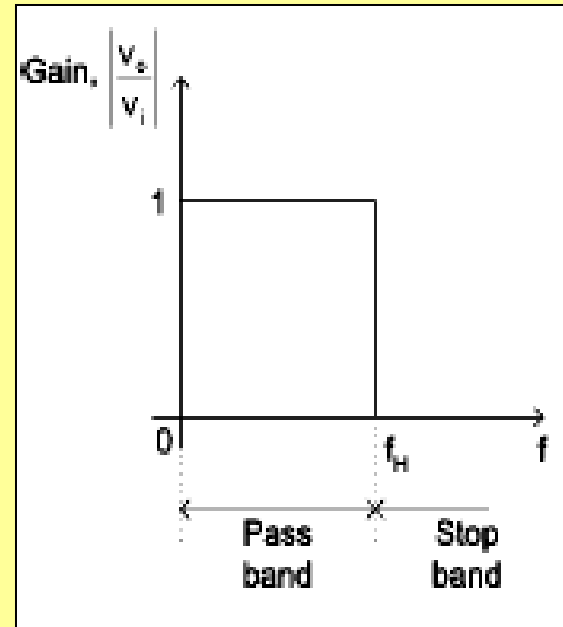


Ideal response

- Ideally, the response drops abruptly at the critical frequency, f_H


Passband of a filter is the range of frequencies that are allowed to pass through the filter with minimum attenuation (usually defined as less than -3 dB of attenuation).

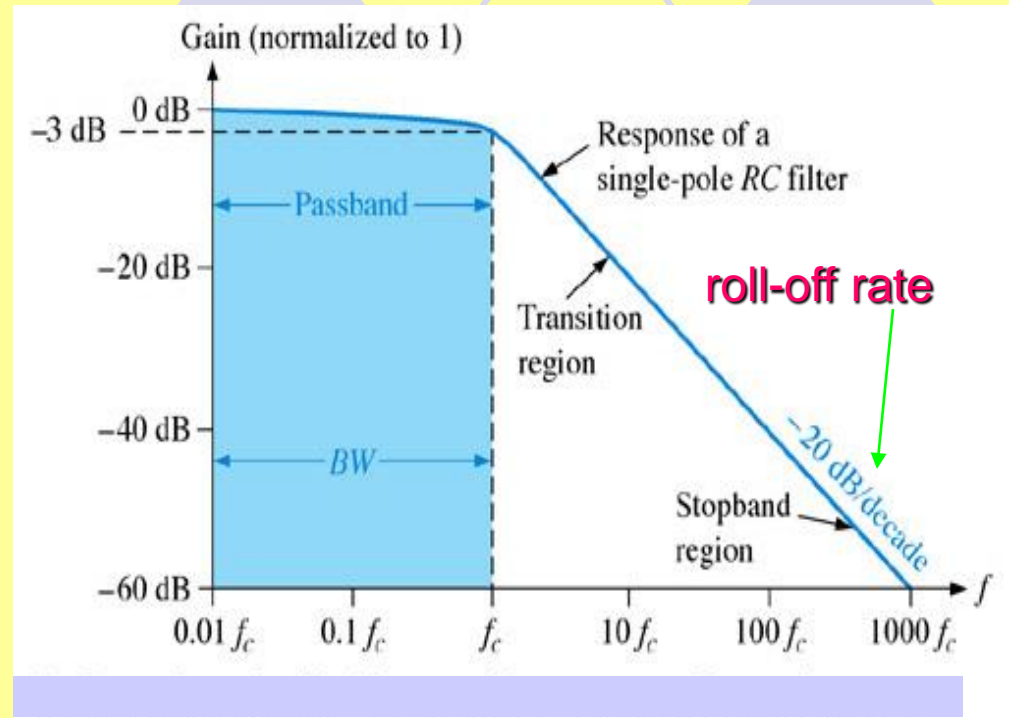Transition region shows the area where the fall-off occurs.




Stopband is the range of frequencies that have the most attenuation.

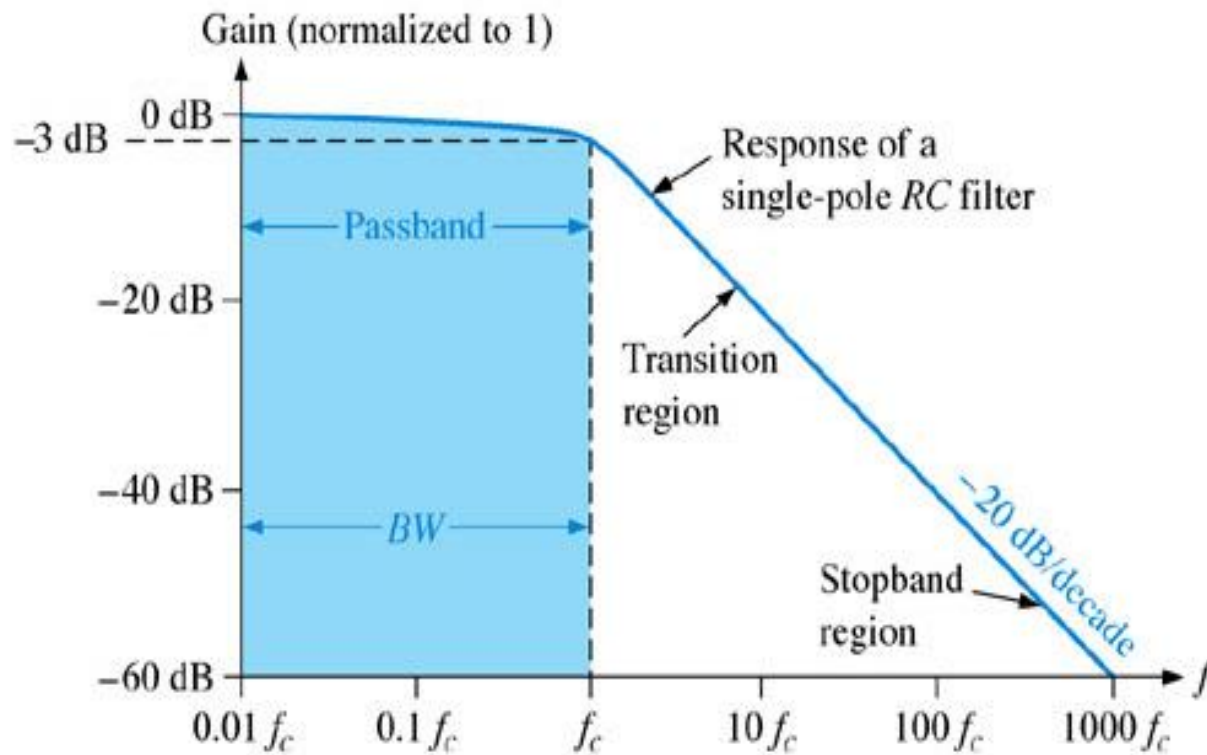Critical frequency, f_c , (also called the cutoff frequency) defines the end of the passband and normally specified at the point where the response drops - 3 dB (70.7%) from the passband response.



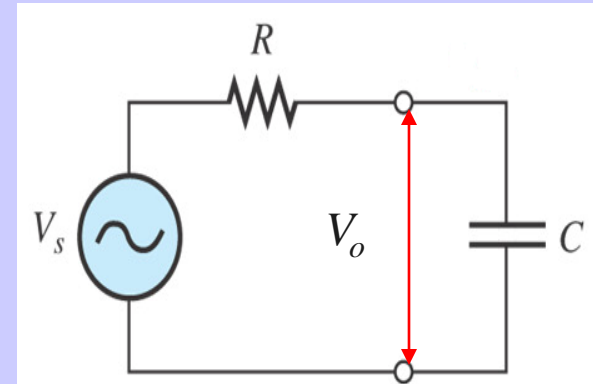(a) Comparison of an ideal low-pass filter response with actual response



(b) Basic low-pass circuit

- At low frequencies, X_C is very high and the capacitor circuit can be considered as open circuit. Under this condition, $V_o = V_{in}$ or $A_V = 1$ (unity).
- At very high frequencies, X_C is very low and the V_o is small as compared with V_{in} . Hence the gain falls and drops off gradually as the frequency is increased.

- The **bandwidth** of an **ideal** low-pass filter is equal to **f_c** :


$$BW = f_c$$

- The critical frequency of a low-pass RC filter occurs when **$X_c = R$** and can be calculated using the formula below:


$$f_c = \frac{1}{2\pi RC}$$

High-Pass Filter Response

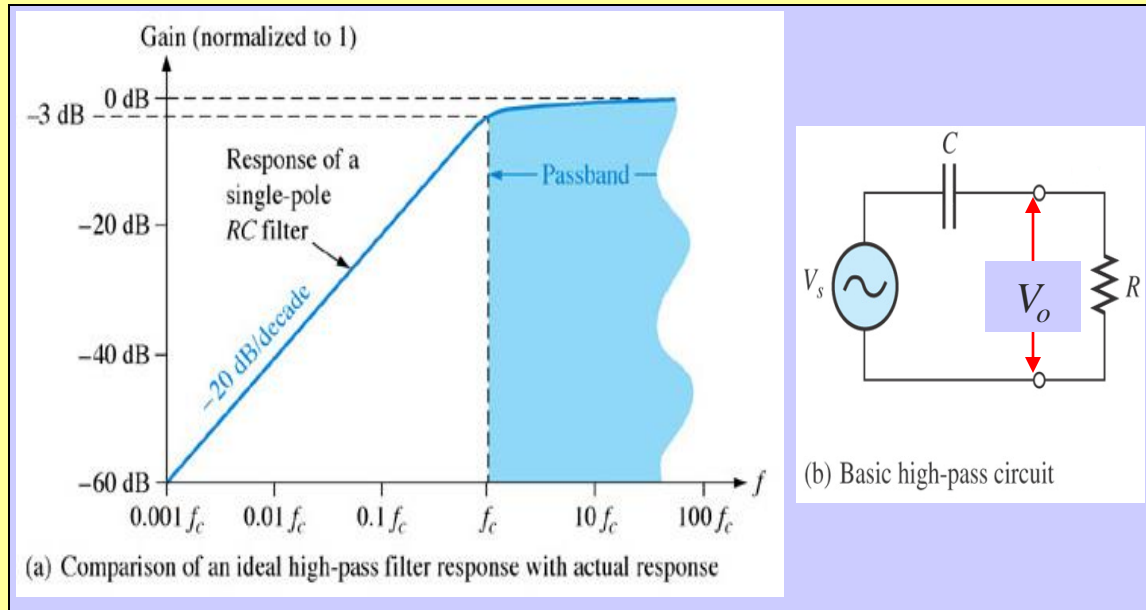- A **high-pass filter** is a filter that significantly attenuates or rejects all frequencies **below** f_c and passes all frequencies **above** f_c .
- The passband of a high-pass filter is all frequencies above the critical frequency.




Actual response

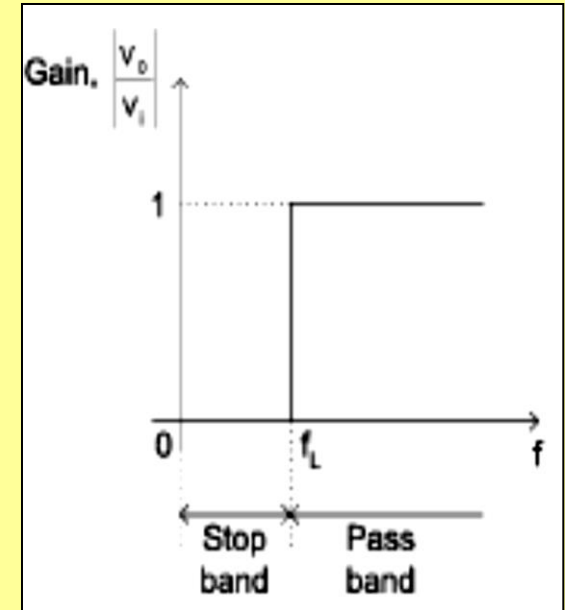

Ideal response


- Ideally, the response rises abruptly at the critical frequency, f_L

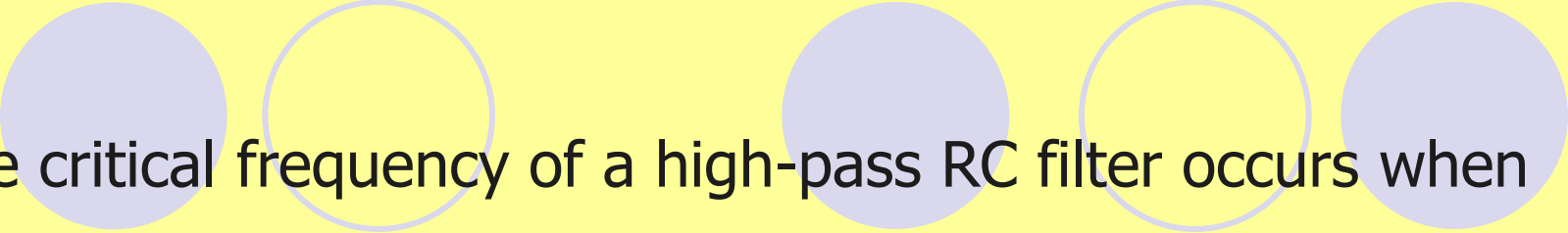- 
- The critical frequency of a high-pass RC filter occurs when **$X_c = R$** and can be calculated using the formula below:


$$f_c = \frac{1}{2\pi RC}$$

Band-Pass Filter Response

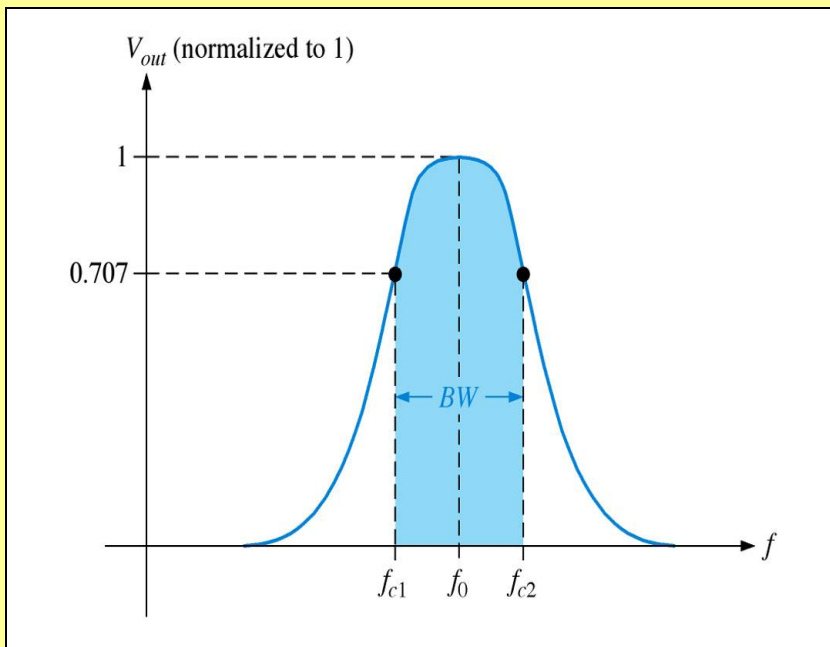
- A **band-pass filter** passes all signals lying within a band between a **lower-frequency limit** and **upper-frequency limit** and essentially rejects all other frequencies that are outside this specified band.



Actual response

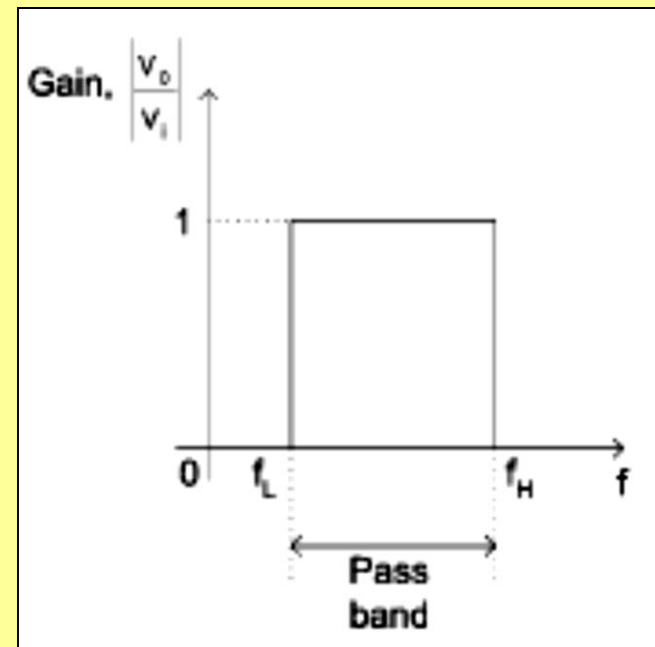


Ideal response

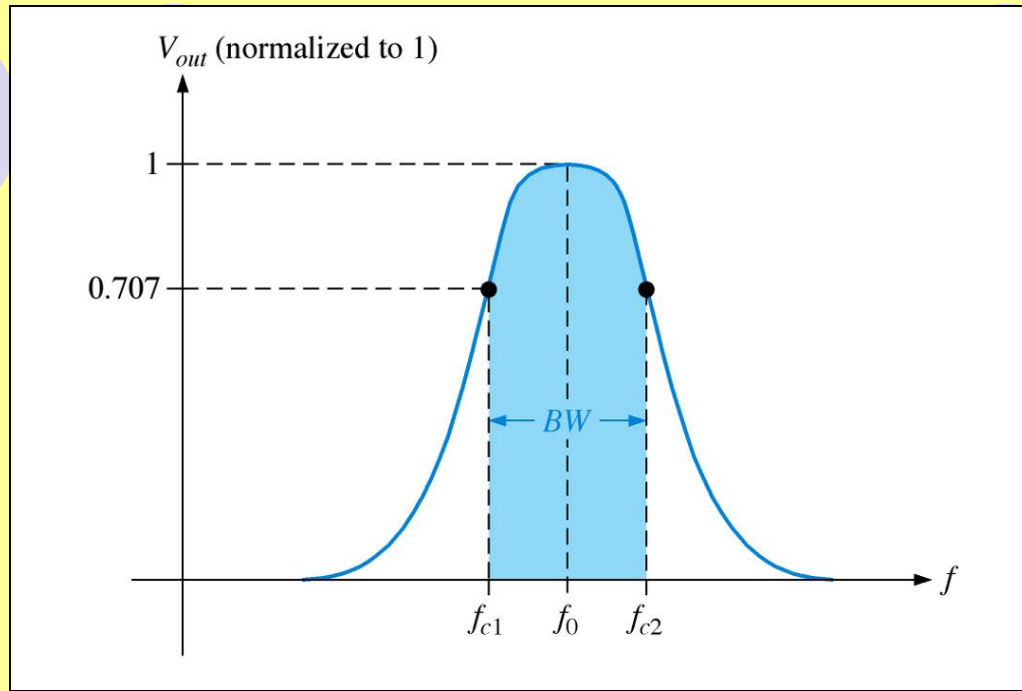

➤ The **bandwidth (BW)** is defined as the **difference** between the **upper critical frequency (f_{c2})** and the **lower critical frequency (f_{c1})**.

$$BW = f_{c2} - f_{c1}$$



➤ The frequency about which the pass band is centered is called the ***center frequency, f_o*** and defined as the geometric mean of the critical frequencies.

$$f_o = \sqrt{f_{c1}f_{c2}}$$


- The **quality factor (Q)** of a band-pass filter is the ratio of the center frequency to the bandwidth.

$$Q = \frac{f_o}{BW}$$


- The higher value of Q , the narrower the bandwidth and the better the selectivity for a given value of f_o .
- ($Q > 10$) as a narrow-band or ($Q < 10$) as a wide-band
- The quality factor (Q) can also be expressed in terms of the damping factor (DF) of the filter as :

$$Q = \frac{1}{DF}$$

Band-Stop Filter Response

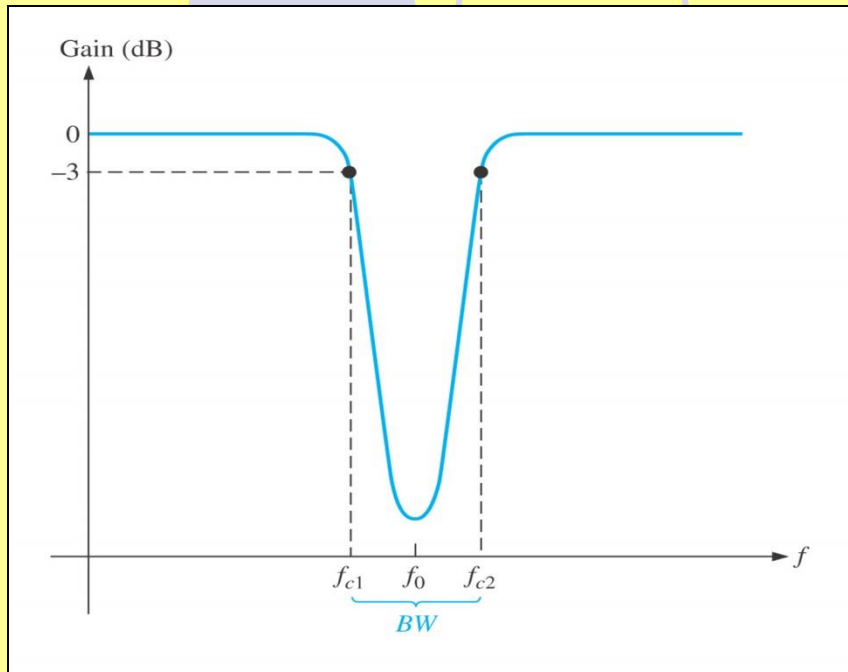

Actual response

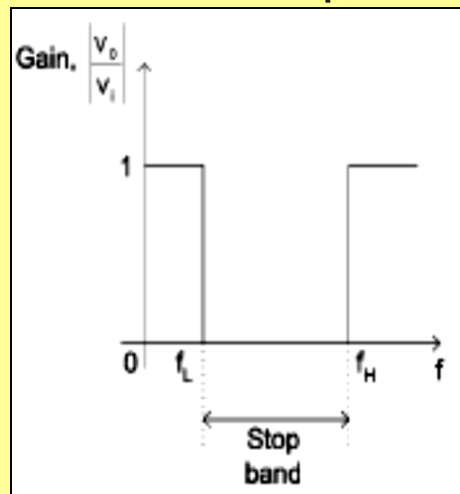

Ideal response


➤ **Band-stop filter** is a filter which its operation is **opposite** to that of the band-pass filter because the frequencies **within** the bandwidth are **rejected**, and the frequencies above f_{c1} and f_{c2} are **passed**.

➤ For the band-stop filter, the **bandwidth** is a band of frequencies between the 3 dB points, just as in the case of the band-pass filter response.

FILTER RESPONSE CHARACTERISTICS

➤ There are **3** characteristics of filter response :

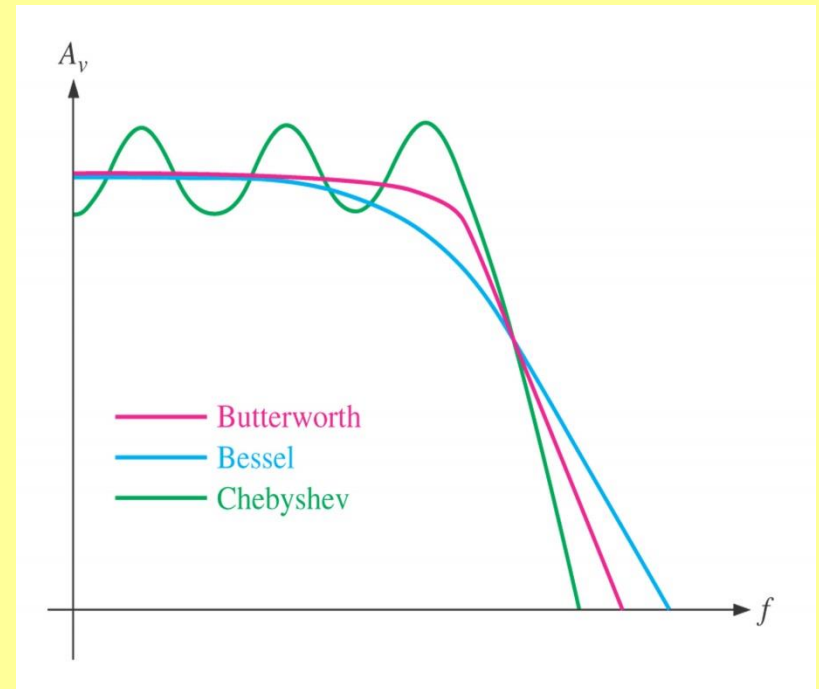- i) **Butterworth** characteristic
- ii) **Chebyshev** characteristic
- iii) **Bessel** characteristic.




Comparative plots of three types of filter response characteristics.

➤ Each of the characteristics is identified by the **shape of the response curve**


Butterworth Characteristic

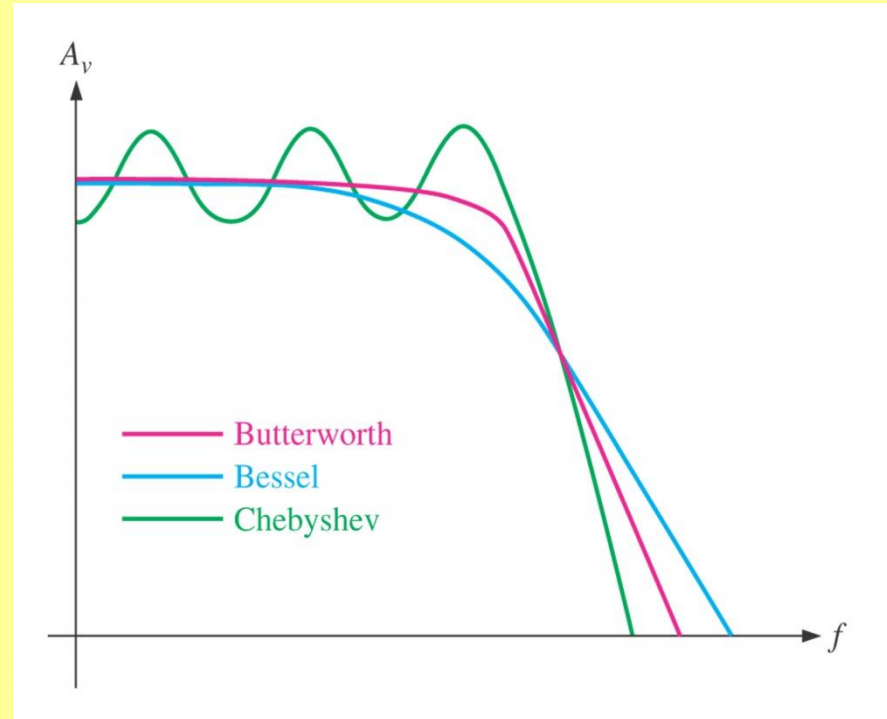- Filter response is characterized by **flat amplitude response** in the passband.
- Provides a roll-off rate of -20 dB/decade/pole.
- Filters with the Butterworth response are normally used when all frequencies in the passband must have the **same gain**.




Chebyshev Characteristic

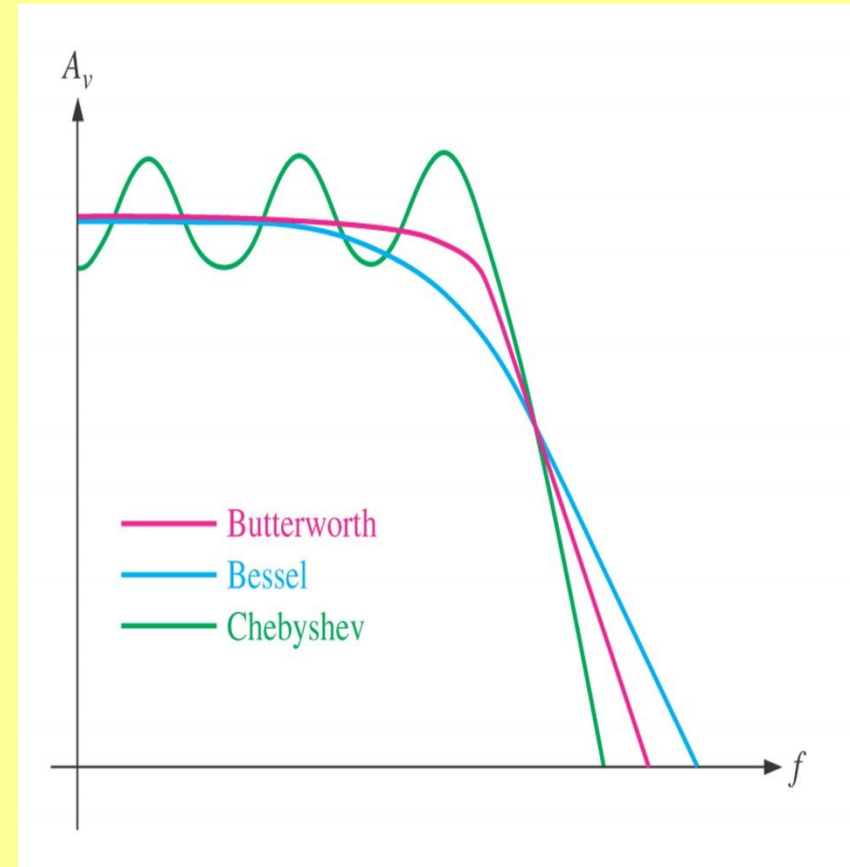- Filter response is characterized by **overshoot** or **ripples** in the passband.
- Provides a roll-off rate greater than -20 dB/decade/pole.
- Filters with the Chebyshev response can be implemented with **fewer poles** and **less complex circuitry** for a given roll-off rate



Bessel Characteristic

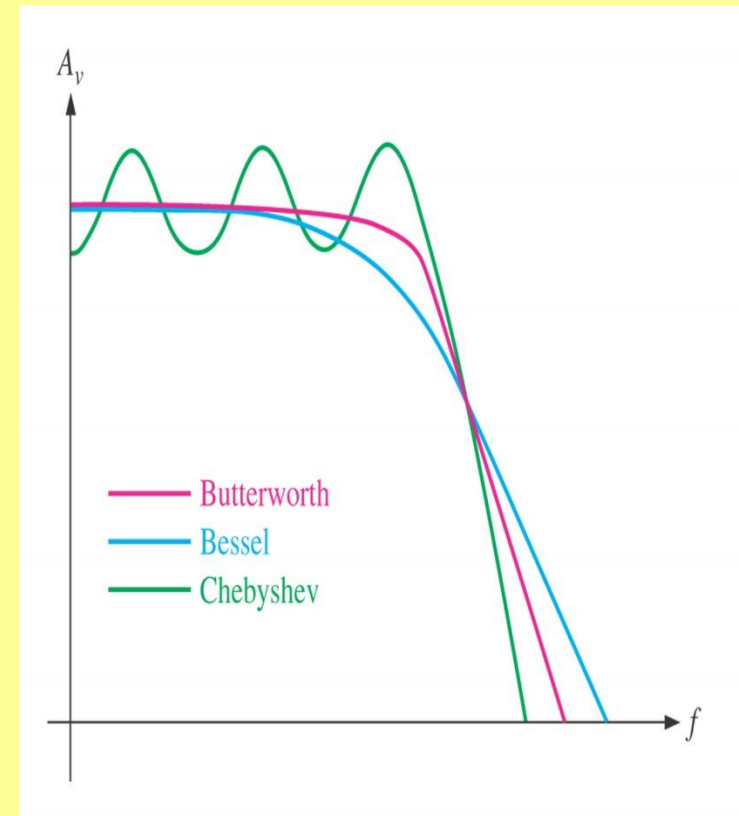- Filter response is characterized by a **linear characteristic**, meaning that the phase shift increases linearly with frequency.
- Filters with the Bessel response are used for filtering pulse waveforms without distorting the shape of waveform.



DAMPING FACTOR


➤ The **damping factor (DF)** of an active filter determines which response characteristic the filter exhibits.

➤ This active filter consists of **an amplifier, a negative feedback circuit** and **RC circuit**.


➤ The amplifier and feedback are connected in a **non-inverting configuration**.

➤ DF is determined by the negative feedback and defined as :


$$DF = 2 - \frac{R_1}{R_2}$$

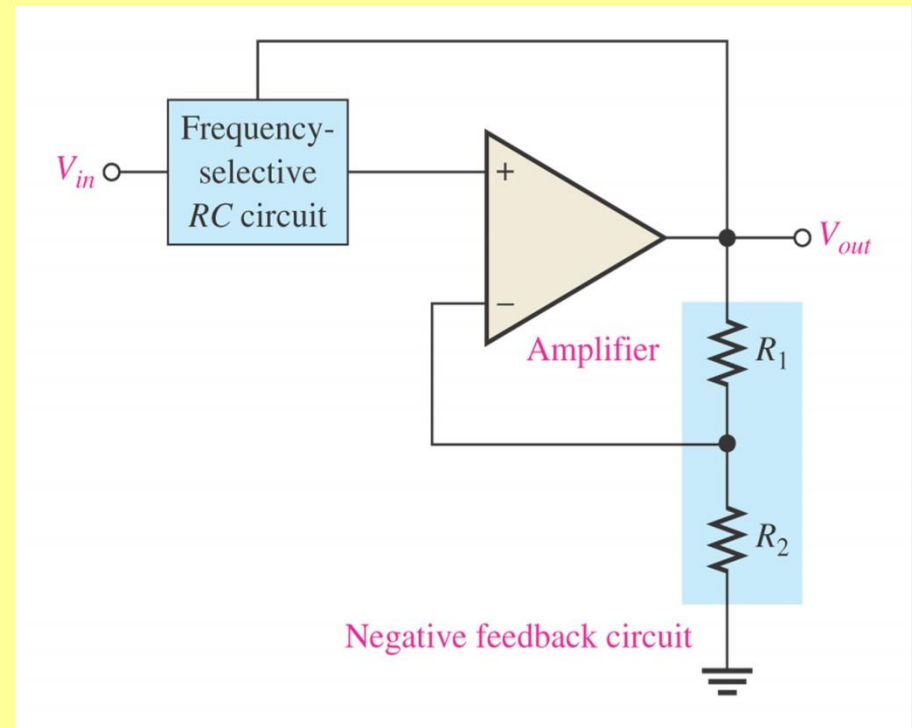

General diagram of active filter


- 
- The value of DF required to produce a desired response characteristics depends on **order** (number of poles) of the filter.
 - A pole (single pole) is simply **one resistor** and **one capacitor**.
 - The **more poles** filter has, the faster its roll-off rate

CRITICAL FREQUENCY AND ROLL-OFF RATE

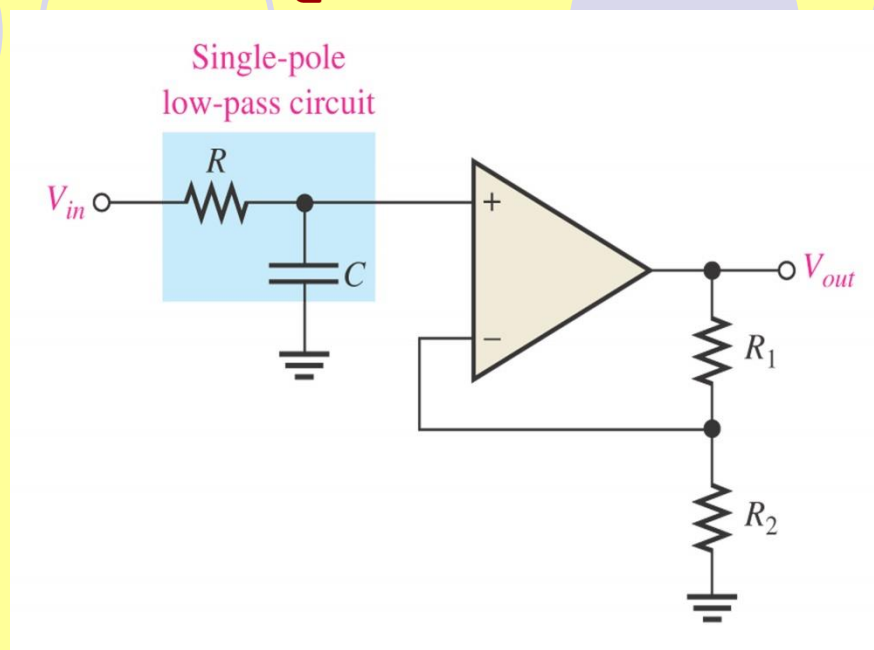

One-pole (first-order) low-pass filter.

- The **critical frequency, f_c** is determined by the values of **R** and **C** in the frequency-selective RC circuit.
- Each **RC** set of filter components represents a **pole**.
- **Greater roll-off rates** can be achieved with **more poles**.
- Each pole represents a **-20dB/decade** increase in roll-off.


- 
- For a single-pole (first-order) filter, the critical frequency is :

$$f_c = \frac{1}{2\pi RC}$$


- The above formula can be used for both low-pass and high-pass filters.

➤ The number of poles determines the roll-off rate of the filter. For example, a Butterworth response produces -20dB/decade/pole. This means that:

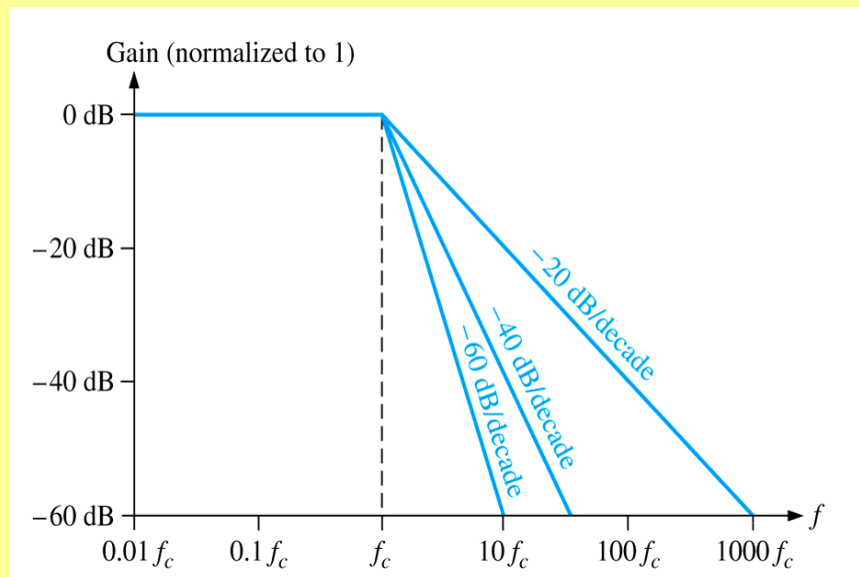- **One-pole (first-order)** filter has a roll-off of -20 dB/decade
- **Two-pole (second-order)** filter has a roll-off of -40 dB/decade
- **Three-pole (third-order)** filter has a roll-off of -60 dB/decade



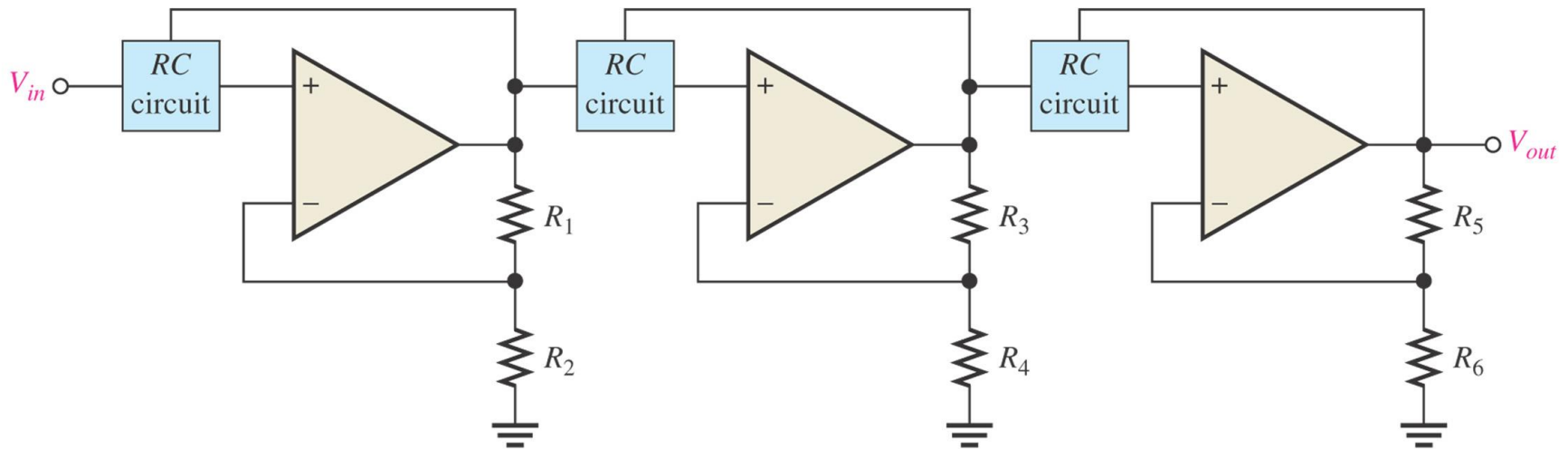➤ The number of filter poles can be increased by *cascading*. To obtain a filter with three poles, cascade a two-pole with one-pole filters.




Three-pole (third-order) low-pass filter.

ACTIVE LOW-PASS FILTERS

Advantages of active filters over passive filters (R, L, and C elements only):

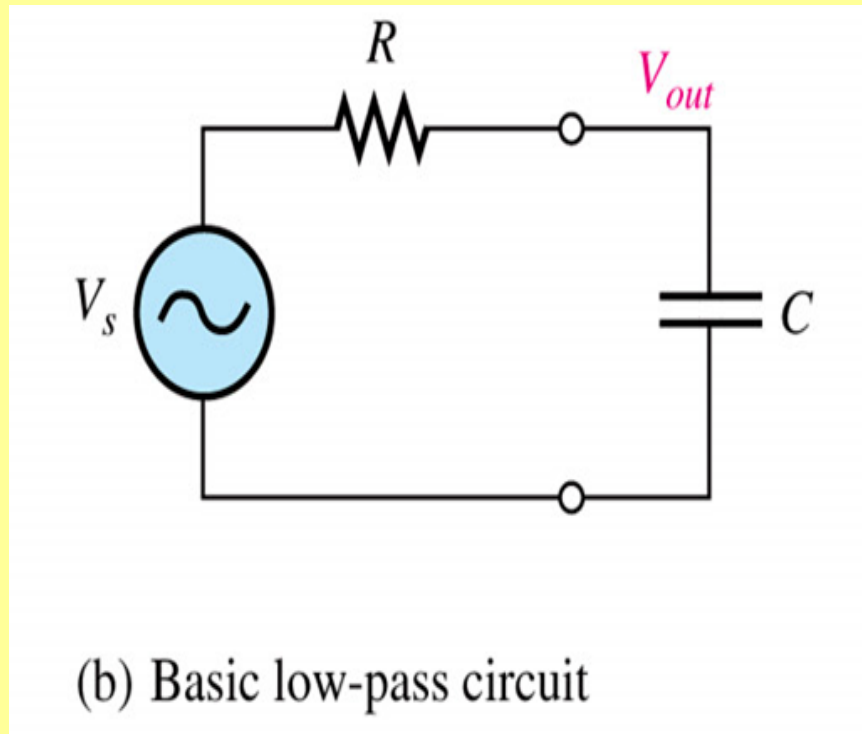1. By containing the op-amp, active filters can be designed to provide required gain, and hence **no signal attenuation** as the signal passes through the filter.
2. **No loading problem**, due to the high input impedance of the op-amp prevents excessive loading of the driving source, and the low output impedance of the op-amp prevents the filter from being affected by the load that it is driving.
3. **Easy to adjust over a wide frequency range** without altering the desired response.

➤ Figure below shows the basic Low-Pass filter circuit



At critical frequency,

Resistance = Capacitance

$$R = X_c$$


$$R = \frac{1}{\omega_c C}$$

$$R = \frac{1}{2\pi f_c C}$$


So, critical frequency ;

$$f_c = \frac{1}{2\pi RC}$$

Single-Pole Filter

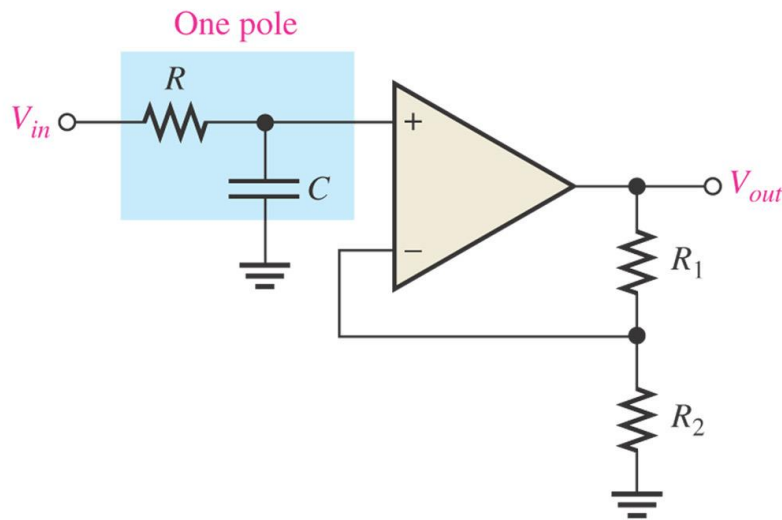

(a)

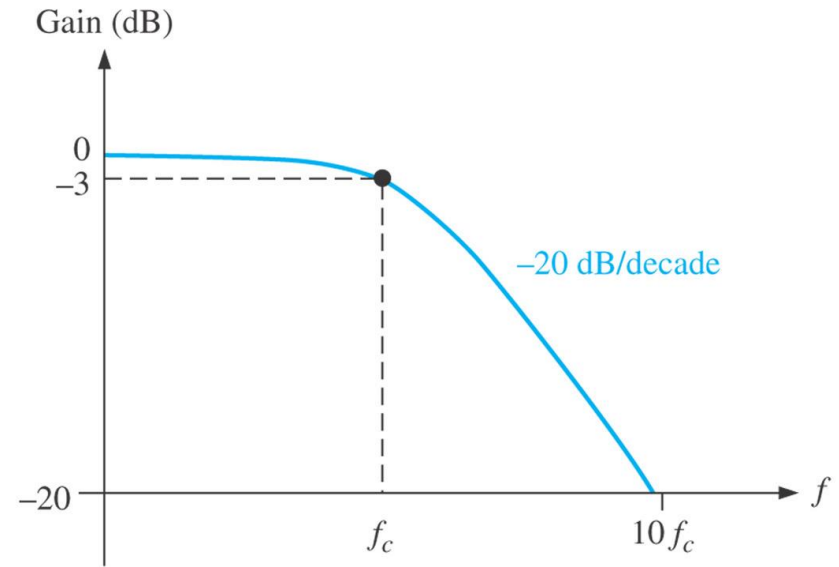

(b)

Single-pole active low-pass filter and response curve.

- This filter provides a roll-off rate of -20 dB/decade above the critical frequency.

➤ The op-amp in single-pole filter is connected as a noninverting amplifier with the closed-loop voltage gain in the passband is set by the values of R_1 and R_2 :


$$A_{cl(NI)} = \frac{R_1}{R_2} + 1$$

➤ The critical frequency of the single-pole filter is :

$$f_c = \frac{1}{2\pi RC}$$

Sallen-Key Low-Pass Filter

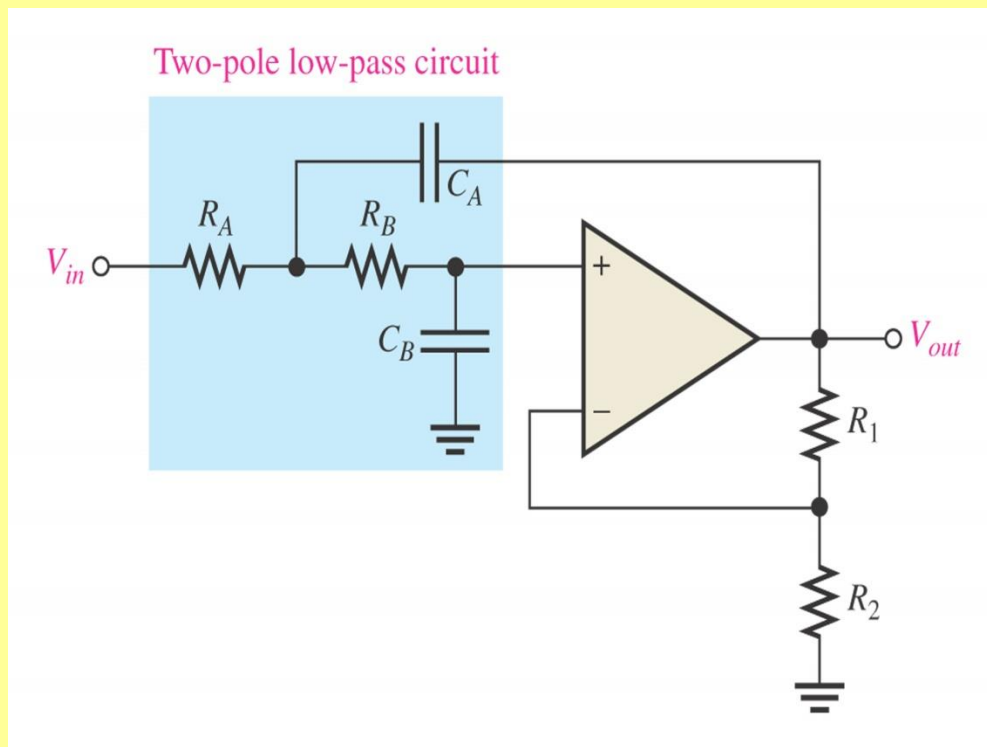- **Sallen-Key** is one of the most common configurations for a **second order** (two-pole) filter.



- There are two low-pass RC circuits that provide a **roll-off of -40 dB/decade above f_c** (assuming a Butterworth characteristics).
- One RC circuit consists of **R_A and C_A** , and the second circuit consists of **R_B and C_B** .

Basic Sallen-Key low-pass filter.

➤ The critical frequency for the Sallen-Key filter is :


$$f_c = \frac{1}{2\pi\sqrt{R_A R_B C_A C_B}}$$

➤ For $R_A = R_B = R$ and $C_A = C_B = C$, thus the critical frequency :

$$f_c = \frac{1}{2\pi RC}$$

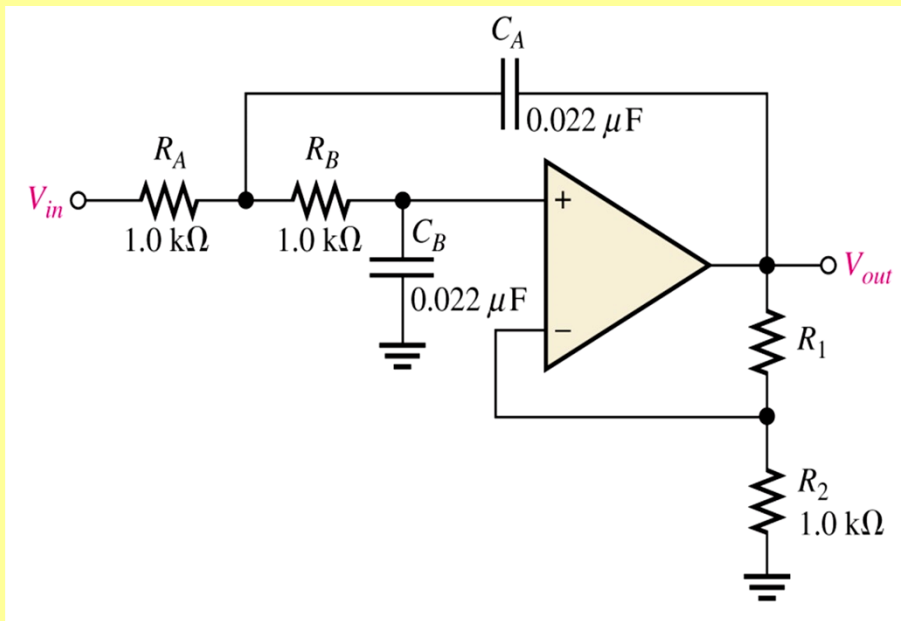Example:

- Determine critical frequency
- Set the value of R_1 for Butterworth response by giving that Butterworth response for second order is 0.586



- Critical frequency

$$f_c = \frac{1}{2\pi RC} = 7.23 \text{ kHz}$$


- Butterworth response given $R_1/R_2 = 0.586$

$$R_1 = 0.586 R_2$$

$$R_1 = 586 \text{ k}\Omega$$


Cascading Low-Pass Filter

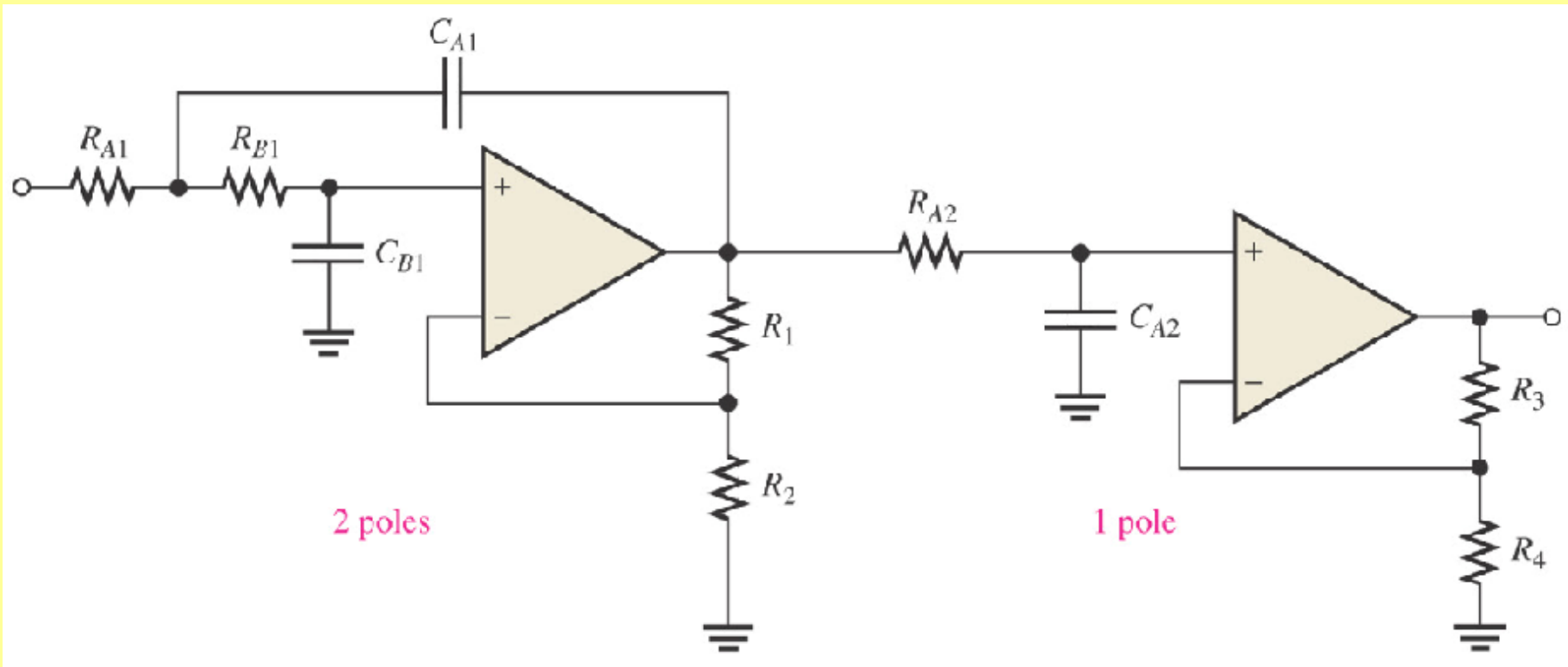- A three-pole filter is required to provide a roll-off rate of **-60 dB/decade**. This is done by cascading a **two-pole Sallen-Key low-pass filter** and a **single-pole low-pass filter**.



Cascaded low-pass filter: third-order configuration.

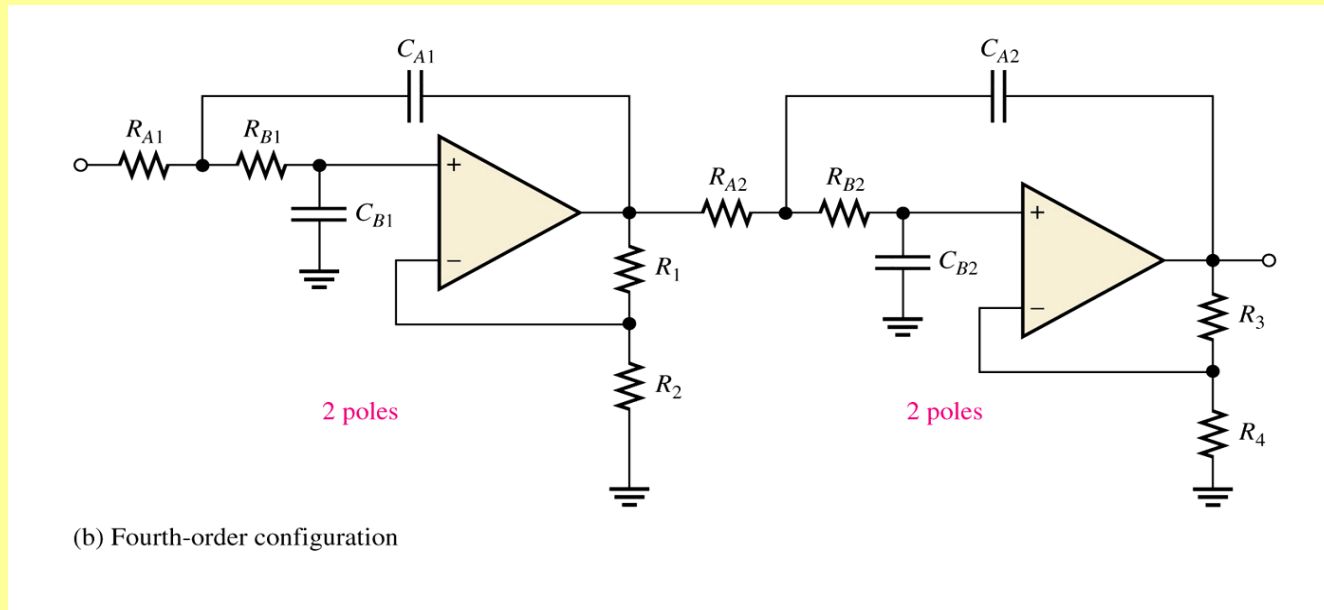
➤ A **four-pole filter** is required to provide a roll-off rate of **-80 dB/decade**. This is done by cascading a **two-pole Sallen-Key low-pass filter** and a **two-pole Sallen-Key low-pass filter**.



Cascaded low-pass filter: fourth-order configuration.

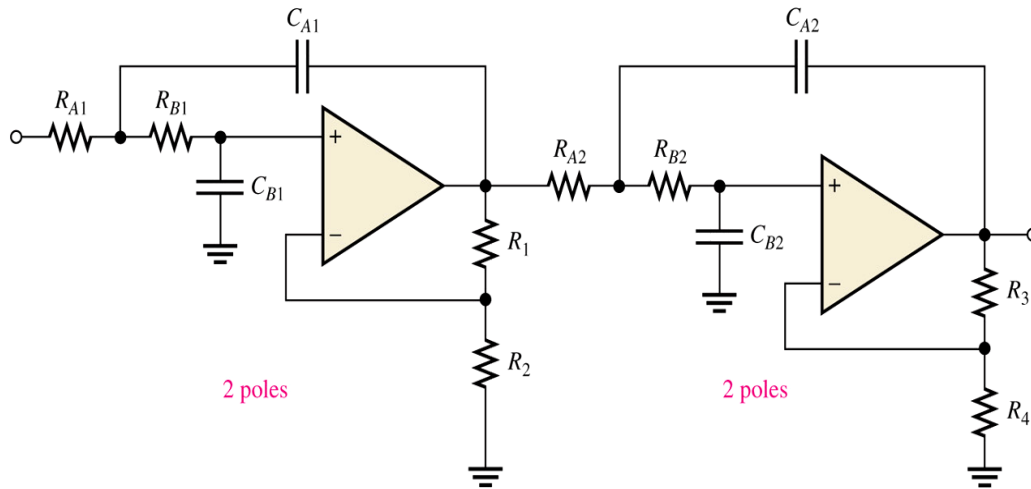Example:

- Determine the capacitance values required to produce a critical frequency of 2680 Hz if all resistors in RC low pass circuit is $1.8\text{k}\Omega$



(b) Fourth-order configuration

$$f_c = \frac{1}{2\pi RC}$$


$$C = \frac{1}{2\pi f_c R} = 0.033\mu F$$

$$C_{A1} = C_{B1} = C_{A2} = C_{B2} = 0.033\mu f$$

- Both stages must have the same f_c . Assume equal-value of capacitor

ACTIVE HIGH-PASS FILTERS

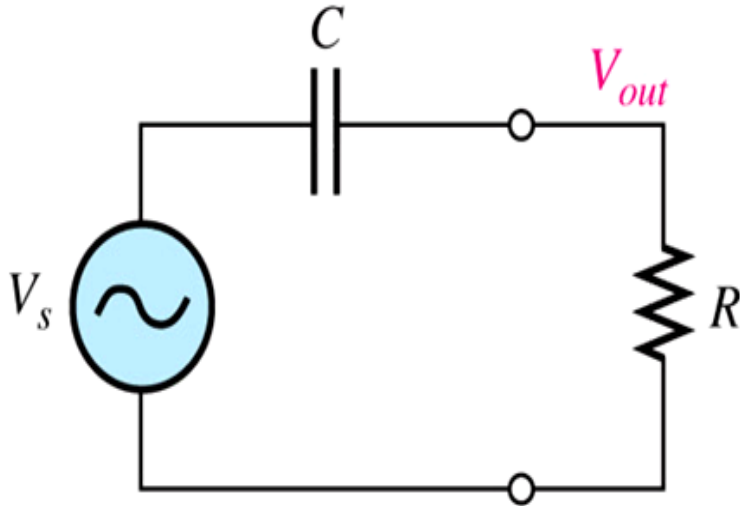- Figure below shows the basic High-Pass filter circuit :



(b) Basic high-pass circuit

At critical frequency,

Resistance = Capacitance

$$R = X_c$$

$$R = \frac{1}{\omega_c C}$$


$$R = \frac{1}{2\pi f_c C}$$

So, critical frequency ;


$$f_c = \frac{1}{2\pi RC}$$

Single-Pole Filter

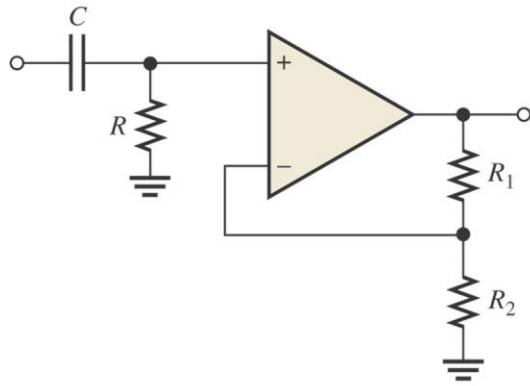- In high-pass filters, the roles of the **capacitor** and **resistor** are **reversed** in the RC circuits as shown from Figure (a). The negative feedback circuit is the same as for the low-pass filters.
- Figure (b) shows a high-pass active filter with a -20dB/decade roll-off



(a)

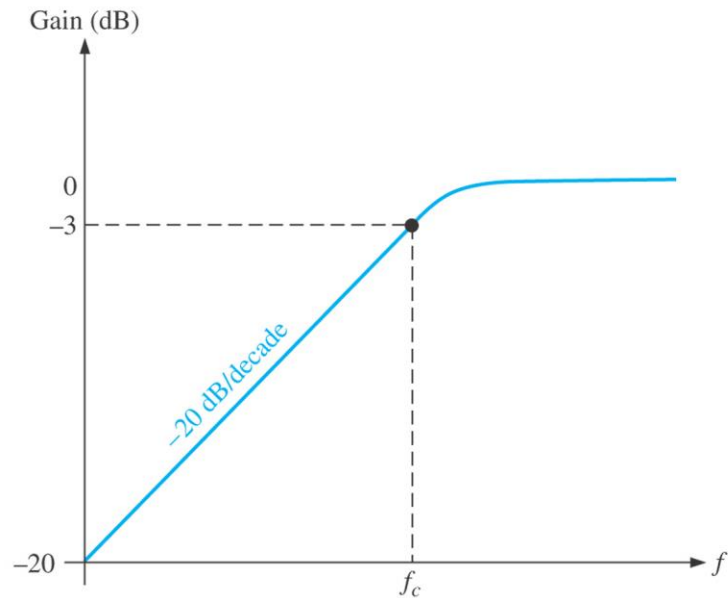

(b)

Single-pole active high-pass filter and response curve.

➤ The op-amp in single-pole filter is connected as a noninverting amplifier with the closed-loop voltage gain in the passband is set by the values of R_1 and R_2 :


$$A_{cl(NI)} = \frac{R_1}{R_2} + 1$$

➤ The critical frequency of the single-pole filter is :

$$f_c = \frac{1}{2\pi RC}$$

Sallen-Key High-Pass Filter

- Components R_A , C_A , R_B , and C_B form the **second order** (two-pole) frequency-selective circuit.
- The position of the resistors and capacitors in the frequency-selective circuit are **opposite** in low pass configuration.
- There are two high-pass RC circuits that provide a **roll-off of -40 dB/decade above f_c**
- The **response characteristics** can be optimized by proper selection of the **feedback resistors**, R_1 and R_2 .

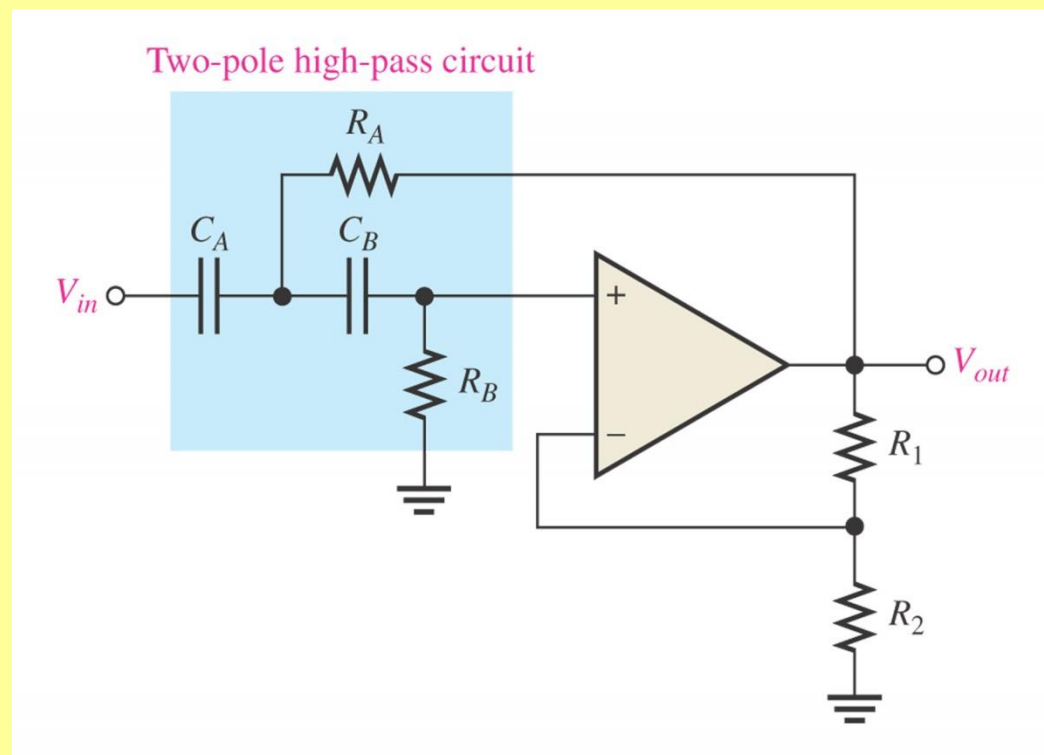

Basic Sallen-Key high-pass filter.

➤ The critical frequency for the Sallen-Key filter is :


$$f_c = \frac{1}{2\pi\sqrt{R_A R_B C_A C_B}}$$

➤ For $R_A = R_B = R$ and $C_A = C_B = C$, thus the critical frequency :

$$f_c = \frac{1}{2\pi RC}$$

Cascading High-Pass Filter

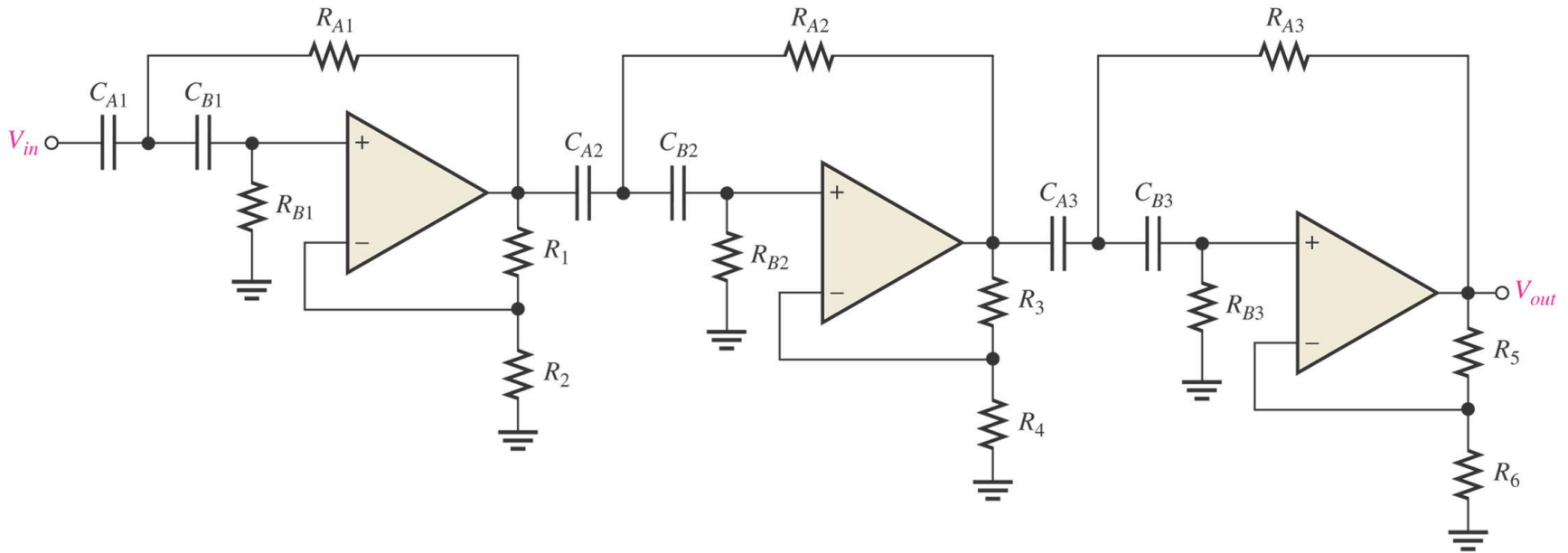
- As with the low-pass filter, first- and second-order high-pass filters can be cascaded to provide three or more poles and thereby create faster roll-off rates.
- A **six-pole high-pass filter** consisting of **three Sallen-Key two-pole** stages with the roll-off rate of **-120 dB/decade**.




Sixth-order high-pass filter

ACTIVE BAND-PASS FILTERS


Cascaded Low-Pass and High-Pass Filters

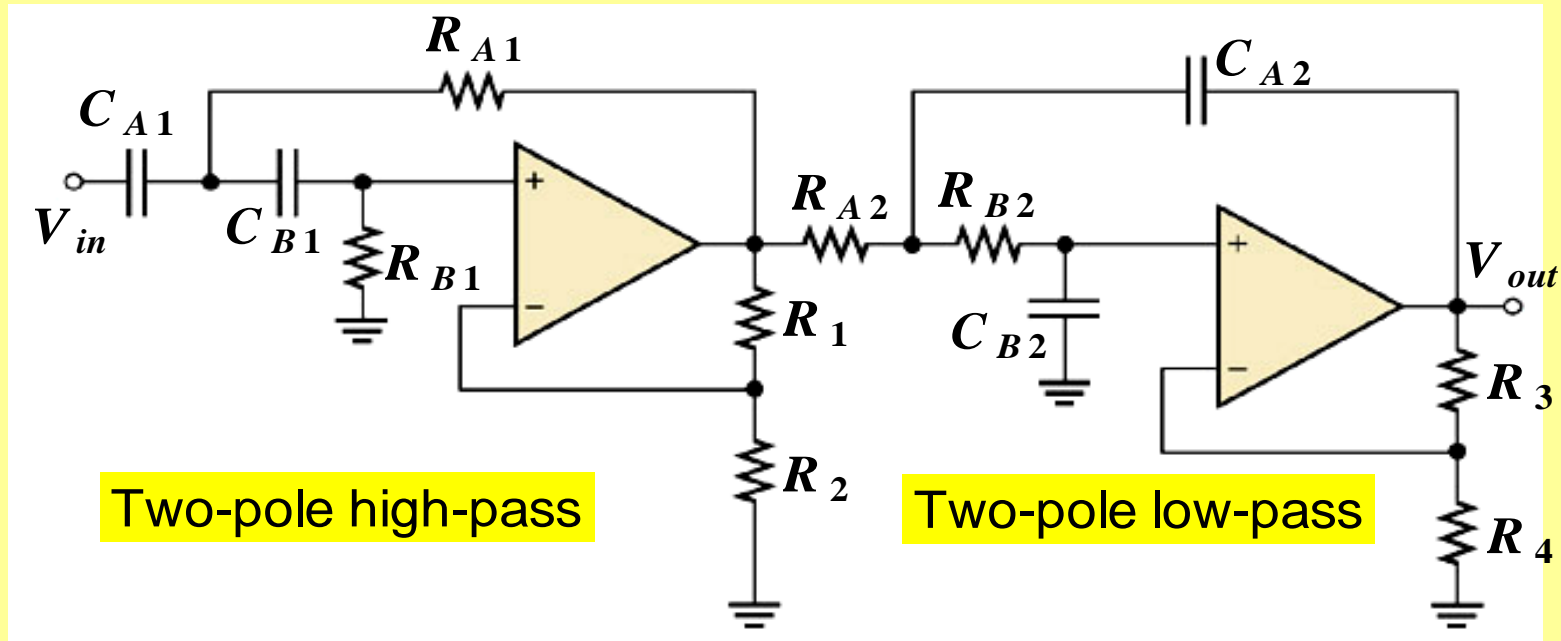

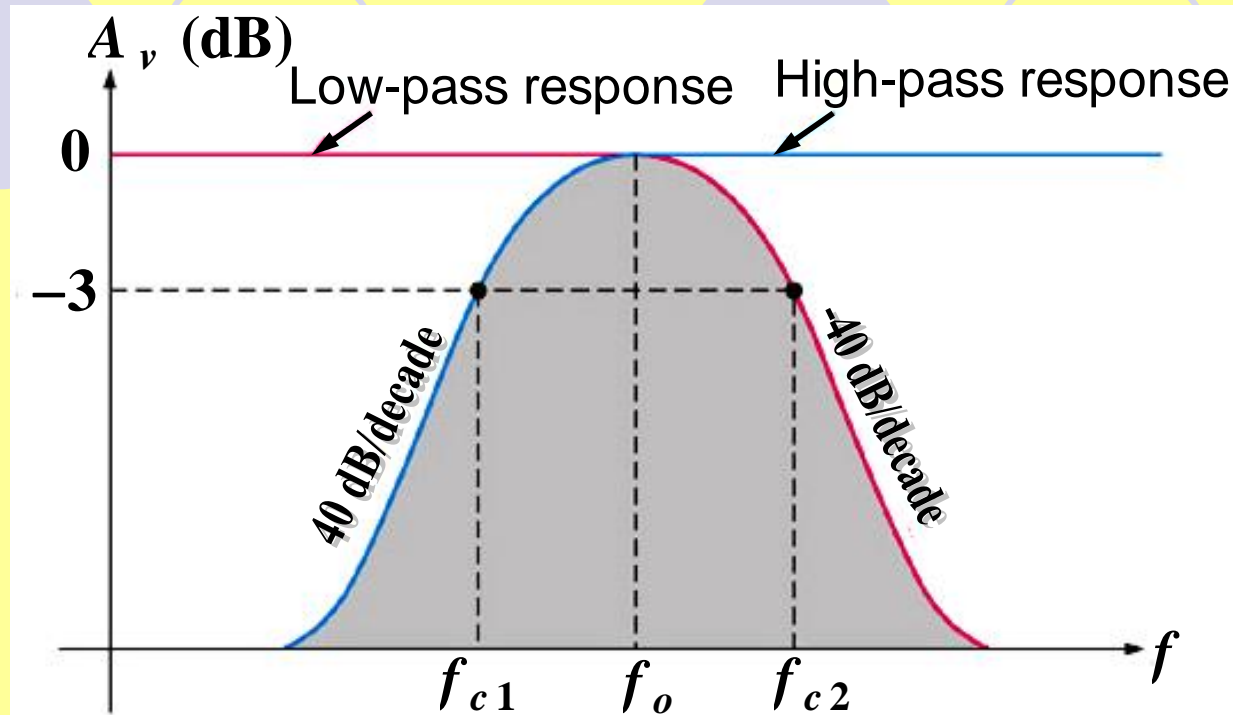- Band-pass filter is formed by cascading a two-pole high-pass and two pole low-pass filter.
- Each of the filters shown is Sallen-Key Butterworth configuration, so that the roll-off rate are -40dB/decade.



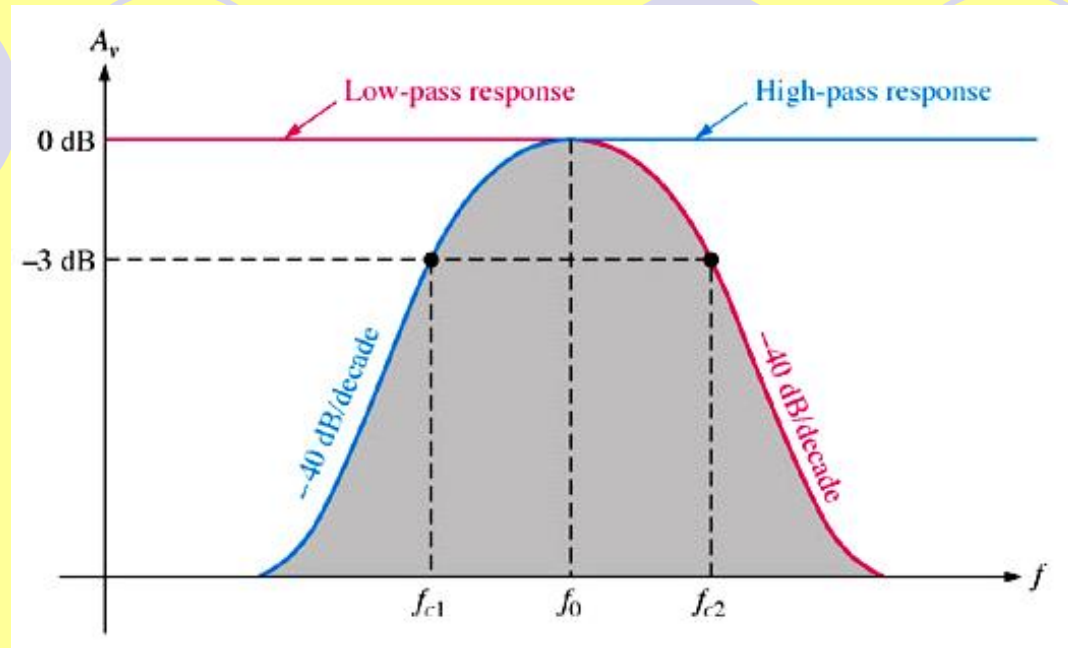- The lower frequency f_{c1} of the passband is the critical frequency of the high-pass filter.
- The upper frequency f_{c2} of the passband is the critical frequency of the low-pass filter.



➤ The following formulas express the three frequencies of the band-pass filter.

$$f_{c1} = \frac{1}{2\pi\sqrt{R_{A1}R_{B1}C_{A1}C_{B1}}}$$


$$f_{c2} = \frac{1}{2\pi\sqrt{R_{A2}R_{B2}C_{A2}C_{B2}}}$$

$$f_0 = \sqrt{f_{c1}f_{c2}}$$

➤ If equal-value components are used in implementing each filter,

$$f_c = \frac{1}{2\pi RC}$$

Multiple-Feedback Band-Pass Filter

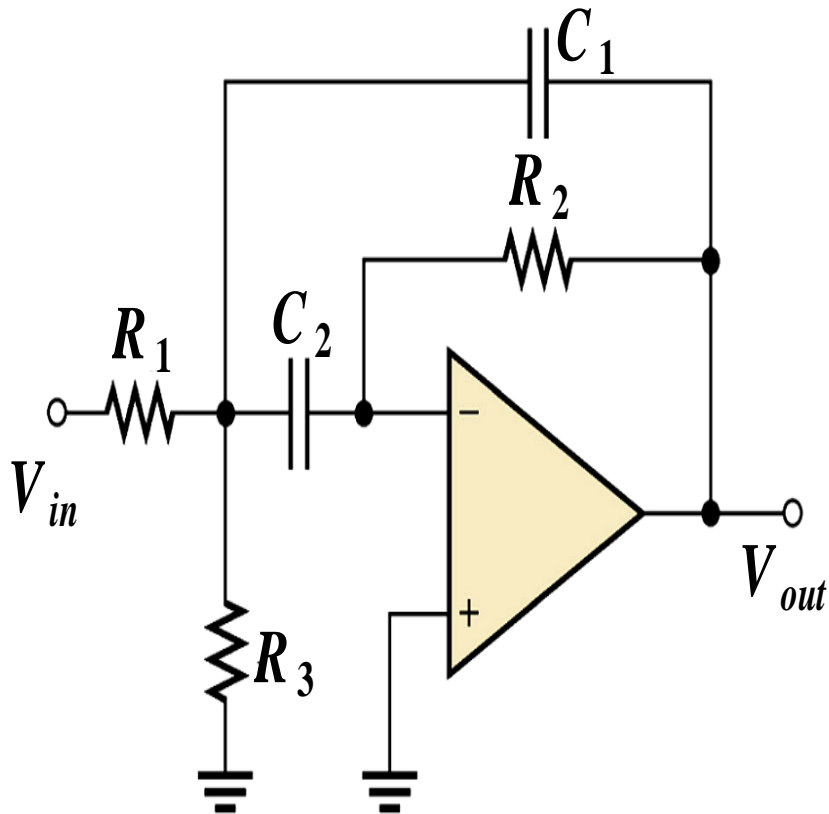

- The low-pass circuit consists of R_1 and C_1 .
- The high-pass circuit consists of R_2 and C_2 .
- The feedback paths are through C_1 and R_2 .
- Center frequency;

$$f_0 = \frac{1}{2\pi\sqrt{(R_1 // R_3)R_2C_1C_2}}$$

- By making $C_1 = C_2 = C$, yields

$$f_0 = \frac{1}{2\pi C} \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3}}$$

- The resistor values can be found by using following formula

$$R_1 = \frac{Q}{2\pi f_o C A_o}$$

$$R_2 = \frac{Q}{\pi f_o C}$$


$$R_3 = \frac{Q}{2\pi f_o C (2Q^2 - A_o)}$$

- The maximum gain, A_o occurs at the center frequency.


$$A_o = \frac{R_2}{2R_1}$$

State-Variable Filter

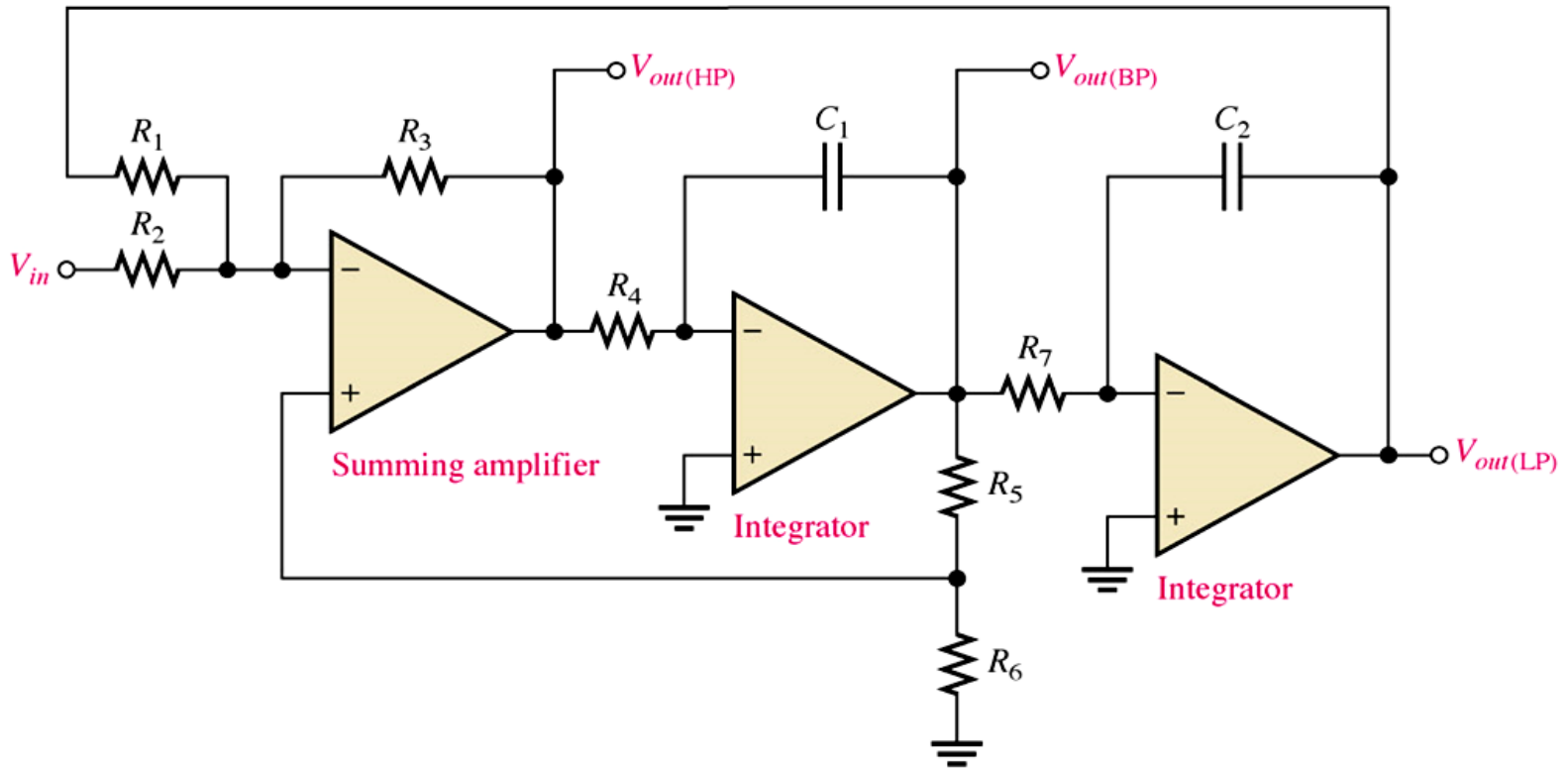
- State-Variable BPF is widely used for band-pass applications.



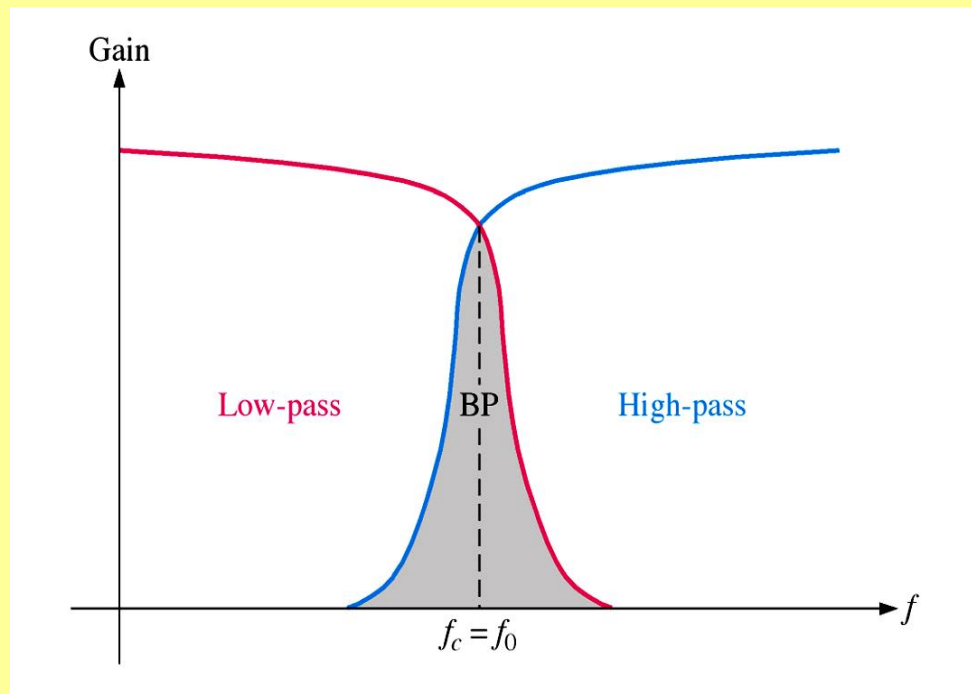- It consists of a summing amplifier and two integrators.
- It has outputs for low-pass, high-pass, and band-pass.
- The center frequency is set by the integrator RC circuits.
- The critical frequency of the integrators usually made equal
- R_5 and R_6 set the Q (bandwidth).



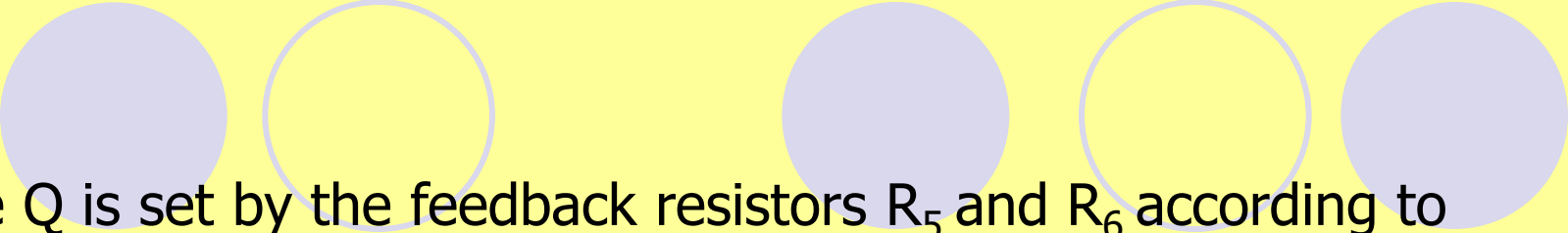- The band-pass output peaks sharply the center frequency giving it a high Q.




➤ The Q is set by the feedback resistors R_5 and R_6 according to the following equations :

$$Q = \frac{1}{3} \left(\frac{R_5}{R_6} + 1 \right)$$

ACTIVE BAND-STOP FILTERS

Multiple-Feedback Band-Stop Filter

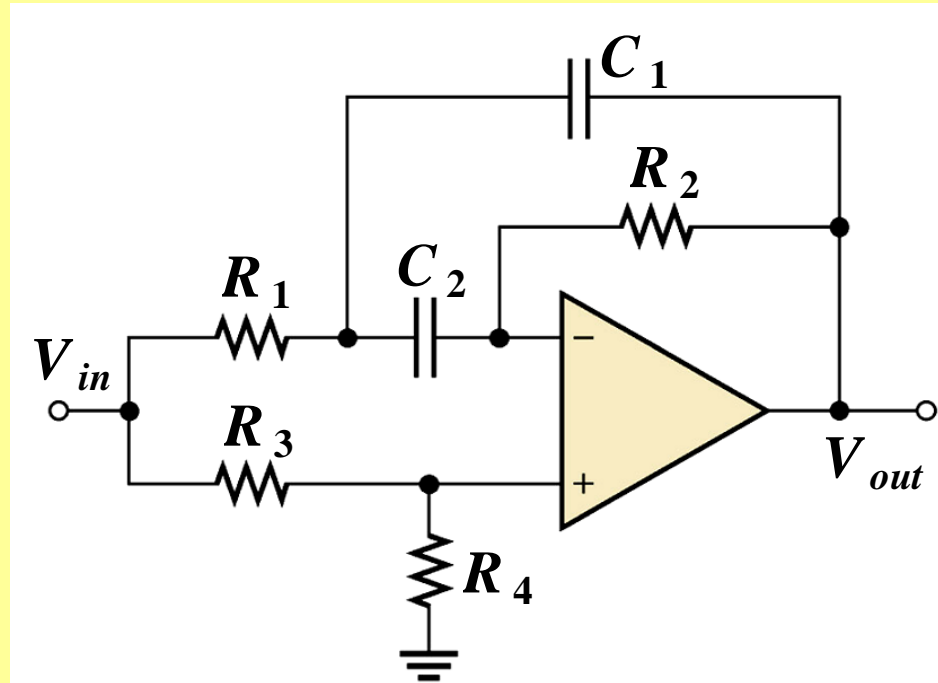

- The configuration is similar to the band-pass version BUT R_3 has been moved and R_4 has been added.
- The BSF is opposite of BPF in that it blocks a specific band of frequencies

FILTER RESPONSE MEASUREMENT


- Measuring frequency response can be performed with typical bench-type equipment.
- It is a process of setting and measuring frequencies both outside and inside the known cutoff points in predetermined steps.
- Use the output measurements to plot a graph.
- More accurate measurements can be performed with sweep generators along with an oscilloscope, a spectrum analyzer, or a scalar analyzer.

SUMMARY

- The bandwidth of a low-pass filter is the same as the upper critical frequency.
- The bandwidth of a high-pass filter extends from the lower critical frequency up to the inherent limits of the circuit.
- The band-pass passes frequencies between the lower critical frequency and the upper critical frequency.



- A band-stop filter rejects frequencies within the upper critical frequency and upper critical frequency.
- The Butterworth filter response is very flat and has a roll-off rate of -20 B
- The Chebyshev filter response has ripples and overshoot in the passband but can have roll-off rates greater than -20 dB

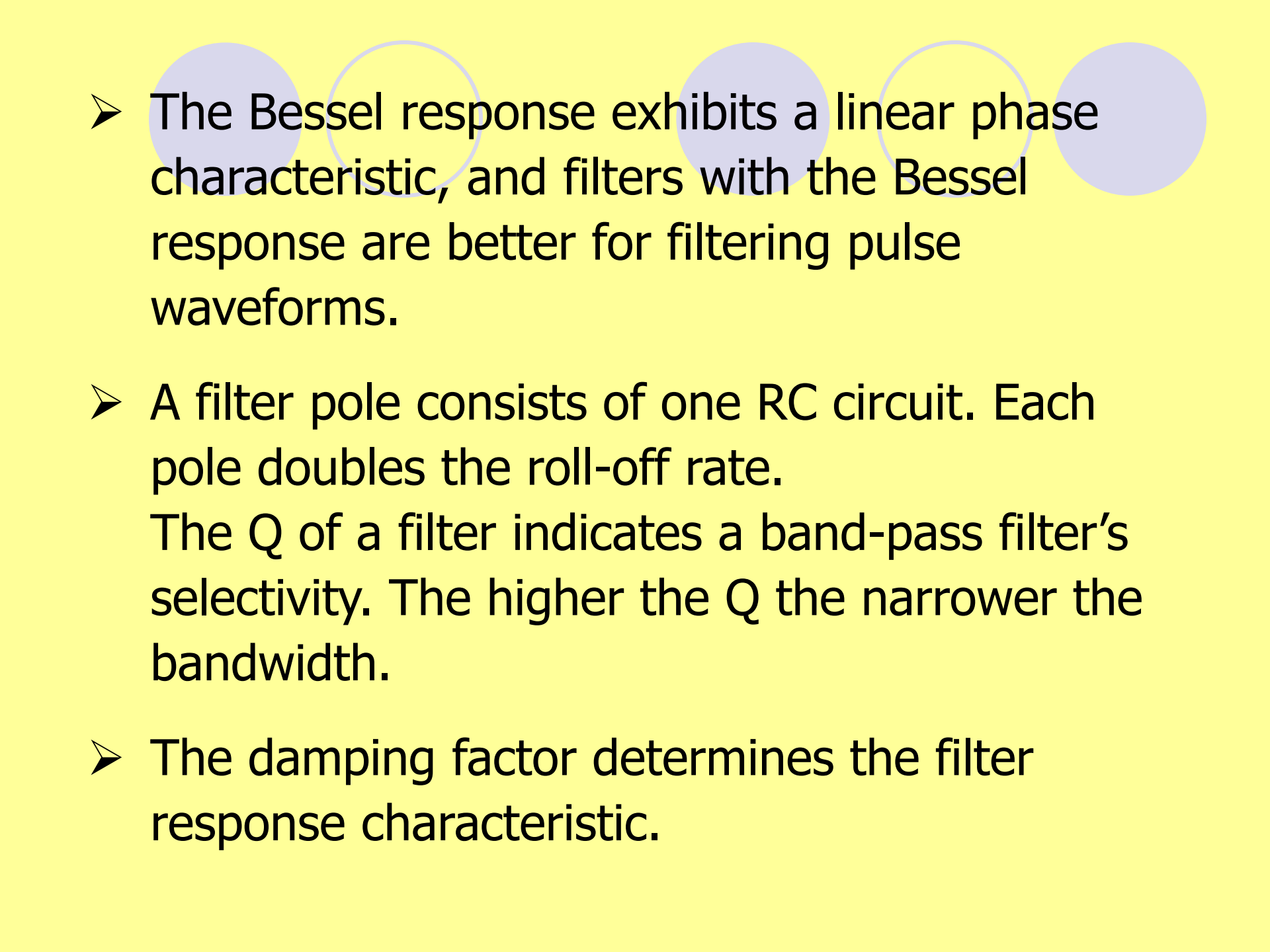- 
- The Bessel response exhibits a linear phase characteristic, and filters with the Bessel response are better for filtering pulse waveforms.
 - A filter pole consists of one RC circuit. Each pole doubles the roll-off rate.
The Q of a filter indicates a band-pass filter's selectivity. The higher the Q the narrower the bandwidth.
 - The damping factor determines the filter response characteristic.